

$$I_D = I_{DSS} \left[ 1 - \frac{V_{GS}}{V_{GS(off)}} \right]^2$$

$$I_D = 12 \left[ 1 + \frac{V_{GS}}{5} \right]^2 \text{ mA}$$

**Example 21.2.** A JFET has the following parameters:  
 $I_{DSS} = 32 \text{ mA}$ ;  $V_{GS(off)} = -8 \text{ V}$ ;  $V_{GS} = -4.5 \text{ V}$ . Find the value of drain current.

**Solution**

$$\begin{aligned} I_D &= I_{DSS} \left[ 1 - \frac{V_{GS}}{V_{GS(off)}} \right]^2 \\ &= 32 \left[ 1 - \frac{(-4.5)}{-8} \right]^2 \text{ mA} \\ &= 6.12 \text{ mA} \end{aligned}$$

 


Fig. 21.14

**Example 21.3.** A JFET has a drain current of  $5 \text{ mA}$ . If  $I_{DSS} = 10 \text{ mA}$  and  $V_{GS(off)} = -6 \text{ V}$ , find the value of (i)  $V_{GS}$  and (ii)  $V_P$ .

**Solution**

$$\begin{aligned} I_D &= I_{DSS} \left[ 1 - \frac{V_{GS}}{V_{GS(off)}} \right]^2 \\ 5 &= 10 \left[ 1 + \frac{V_{GS}}{6} \right]^2 \end{aligned}$$

$$1 + \frac{V_{GS}}{6} = \sqrt{5/10} = 0.707$$

$$\therefore V_{GS} = -1.76 \text{ V}$$

$$\text{and } V_P = -V_{GS(off)} = 6 \text{ V}$$

### 21.11. Advantages of JFET

A JFET is a voltage controlled, constant current device (similar to a vacuum pentode) in which variations in input voltage control the output current. It combines the many advantages of both bipolar transistor and vacuum pentode. Some of the advantages of a JFET are :

(i) It has a very high input impedance (of the order of  $100 \text{ M}\Omega$ ). This permits high degree of isolation between the input and output circuits.

(ii) The operation of a JFET depends upon the bulk material current carriers that do not cross junctions. Therefore, the inherent noise of tubes (due to high-temperature operation) and those of transistors (due to junction transitions) are not present in a JFET.

(iii) A JFET has a negative temperature co-efficient of resistance. This avoids the risk of thermal runaway.

(iv) A JFET has a very high power gain. This eliminates the necessity of using driver stages.

(v) A JFET has a smaller size, longer life and high efficiency.

### 21.12. Parameters of JFET

Like vacuum tubes, a *JFET* has certain parameters which determine its performance in a circuit. The main parameters of a *JFET* are (i) a.c. drain resistance (ii) transconductance (iii) amplification factor.

(i) **a.c. drain resistance ( $r_d$ )**. Corresponding to the a.c. plate resistance, we have a.c. drain resistance in a *JFET*. It may be defined as follows :

It is the ratio of change in drain-source voltage ( $\Delta V_{DS}$ ) to the change in drain current ( $\Delta I_D$ ) at constant gate-source voltage i.e.

$$\text{a.c. drain resistance } r_d = \frac{\Delta V_{DS}}{\Delta I_D} \text{ at constant } V_{GS}$$

For instance, if a change in drain voltage of 2V produces a change in drain current of 0.02mA, then

$$\text{a.c. drain resistance, } r_d = \frac{2V}{0.02mA} = 100k\Omega$$

Referring to the output characteristics of a *JFET* in Fig. 21.8, it is clear that above the pinch off voltage, the change in  $I_D$  is small for a change in  $V_{DS}$  because the curve is almost flat. Therefore, drain resistance of a *JFET* has a large value, ranging from 10k $\Omega$  to 1M $\Omega$ .

(ii) **Transconductance ( $g_{fs}$ )**. The control that the gate voltage has over the drain current is measured by transconductance  $g_{fs}$  and is similar to the transconductance  $g_m$  of the tube. It may be defined as follows :

It is the ratio of change in drain current ( $\Delta I_D$ ) to the change in gate-source voltage ( $\Delta V_{GS}$ ) at constant drain-source voltage i.e.

$$\text{Transconductance, } g_{fs} = \frac{\Delta I_D}{\Delta V_{GS}} \text{ at constant } V_{DS}$$

The transconductance of a *JFET* is usually expressed either in mA/volt or micromhos. As an example, if a change in gate voltage of 0.1V causes a change in drain current of 0.3mA, then,

$$\begin{aligned} \text{Transconductance, } g_{fs} &= \frac{0.3mA}{0.1V} = 3mA/V = 3 \times 10^{-3} A/V \text{ or mho} \\ &= 3 \times 10^{-3} \times 10^6 \mu\text{mhos} = 3000 \mu\text{mhos} \end{aligned}$$

(iii) **Amplification factor ( $\mu$ )**. It is the ratio of change in drain-source voltage ( $\Delta V_{DS}$ ) to the change in gate-source voltage ( $\Delta V_{GS}$ ) at constant drain current i.e.

$$\text{Amplification factor, } \mu = \frac{\Delta V_{DS}}{\Delta V_{GS}} \text{ at constant } I_D$$

Amplification factor of a *JFET* indicates how much more control the gate voltage has over drain current than has the drain voltage. For instance, if the amplification factor of a *JFET* is 50, it means that gate voltage is 50 times as effective as the drain voltage in controlling the drain current.

### 21.13. Relation Among JFET Parameters

The relationship among *JFET* parameters can be established as under :

$$\text{We know } \mu = \frac{\Delta V_{DS}}{\Delta V_{GS}}$$

$$\Delta I_D = 10.25 - 9.65 = 0.6 \text{ mA}$$

$$\therefore \text{Transconductance, } g_{fs} = \frac{\Delta I_D}{\Delta V_{GS}} = \frac{0.6 \text{ mA}}{0.2 \text{ V}} = 3 \text{ mA/V} = 3000 \mu\text{mho}$$

$$\therefore \text{(iii) Amplification factor, } \mu_{fs} = (32 \times 10^3) \times (3000 \times 10^{-6}) = 96$$

## 21.14. JFET Biasing

For the proper operation of *JFET*, gate must be negative w.r.t. source. This can be achieved either by inserting a battery in the gate circuit or by a circuit known as biasing circuit. The latter method is preferred because batteries are costly and require frequent replacement.

**1. Bias battery.** Fig. 21.15 shows the biasing of a *JFET* by a bias battery  $V_{GG}$ . This battery ensures that gate is always negative w.r.t. source during all parts of the signal.

**2. Biasing circuit.** The biasing circuit uses supply voltage  $V_{DD}$  to provide the necessary bias. Two most commonly used methods are (i) self-bias (ii) potential divider method.

**(i) Self-bias.** Fig. 21.16 shows the self-bias method. The resistor  $R_S$  is the bias resistor. The d.c. component of drain current flowing through  $R_S$  produces the desired bias voltage. The capacitor  $C_S$  bypasses the a.c. component of the drain current.

 


Fig. 21.15

 


Fig. 21.16

Voltage across  $R_S$ ,  $V_S = I_D R_S$

Since gate current is negligibly small, the gate terminal is at d.c. ground i.e.,  $V_G = 0$

$$\therefore V_{GS} = V_G - V_S = 0 - I_D R_S$$

or

$$V_{GS} = -I_D R_S$$

Thus bias voltage  $V_{GS}$  keeps gate negative w.r.t. source.

**Operating point.** The operating point (i.e., zero signal  $I_D$  and  $V_{DS}$ ) can be easily determined. Since the parameters of the *JFET* are usually known, zero signal  $I_D$  can be calculated from the following relation :

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

Also  $V_{DS} = V_{DD} - I_D (R_D + R_S)$

Thus d.c. conditions of *JFET* amplifier are fully specified.



(ii) **Potential divider method.** Fig. 21.17 shows potential divider method of biasing a *JFET*. This circuit is identical to that used for a transistor. The resistors  $R_1$  and  $R_2$  form a voltage divider across drain supply  $V_{DD}$ . The voltage  $V_2$  across  $R_2$  provides the necessary bias.

$$V_2 = \frac{V_{DD}}{R_1 + R_2} \times R_2$$

Now

$$V_2 = V_{GS} + I_D R_S$$

or

$$V_{GS} = V_2 - I_D R_S$$

The circuit is so designed that  $I_D R_S$  is larger than  $V_2$  so that  $V_{GS}$  is negative. This provides correct bias voltage. We can find the operating point as under:

$$I_D = \frac{V_2 - V_{GS}}{R_S}$$

and

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

 


Fig. 21.17


### 21.15. JFET Connections

There are three leads in a *JFET* viz., source, gate and drain terminals. However, when *JFET* is to be connected in a circuit, we require four terminals; two for the input and two for the output. This difficulty is overcome by making one terminal of the *JFET* common to both input and output terminals. Accordingly, a *JFET* can be connected in a circuit in the following three ways :

(i) Common source connection

(ii) Common gate connection

(iii) Common drain connection

 

Common source connection

Fig. 21.18

The common source connection is the most widely used arrangement. It is because this connection provides high input impedance, good voltage gain and a moderate output impedance. However, the circuit produces a phase reversal i.e., output signal is  $180^\circ$  out of phase with the input signal. Fig. 21.18 shows a common source *n*-channel JFET amplifier. Note that source terminal is common to both input and output.

**Note.** A common source JFET amplifier is the JFET equivalent of common emitter amplifier. Both amplifiers have a  $180^\circ$  phase shift from input to output. Although the two amplifiers serve the same basic purpose, the means by which they operate are quite different.

**Example 21.7.** In a self-bias *n*-channel JFET, the operating point is to be set at  $I_D = 1.5\text{mA}$  and  $V_{DS} = 10\text{V}$ . The JFET parameters are  $I_{DSS} = 5\text{mA}$ , and  $V_P = -2\text{V}$ . Find the values of  $R_S$  and  $R_D$ . Given that  $V_{DD} = 20\text{V}$ .

**Solution**

Fig. 21.19 shows the circuit arrangement.

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$\text{or} \quad 1.5 = 5 \left( 1 + \frac{V_{GS}}{2} \right)^2$$

$$\text{or} \quad 1 + \frac{V_{GS}}{2} = \sqrt{1.5/5} = 0.55$$

$$\text{or} \quad V_{GS} = -0.9\text{V}$$

$$\text{Now,} \quad V_{GS} = V_G - V_S$$

$$\begin{aligned} \text{or} \quad V_S &= V_G - V_{GS} \\ &= 0 - (-0.9) = 0.9\text{V} \end{aligned}$$

$$\therefore R_S = \frac{V_S}{I_D} = \frac{0.9\text{V}}{1.5\text{mA}} = 0.6\text{K}\Omega$$

Applying Kirchhoff's voltage law to the drain circuit, we have,

$$V_{DD} = I_D R_D + V_{DS} + I_D R_S$$

$$\text{or} \quad 20 = 1.5\text{mA} \times R_D + 10 + 0.9$$

$$\therefore R_D = \frac{(20 - 10 - 0.9)\text{V}}{1.5\text{mA}} = 6\text{K}\Omega$$

**Example 21.8.** In an *n*-channel JFET biased by potential divider method, it is desired to set the operating point at  $I_D = 2.5\text{mA}$  and  $V_{DS} = 8\text{V}$ . If  $V_{DD} = 30\text{V}$ ,  $R_1 = 1\text{M}\Omega$  and  $R_2 = 500\text{K}\Omega$ , find the value of  $R_S$ . The parameters of JFET are  $I_{DSS} = 10\text{mA}$  and  $V_P = -5\text{V}$ .

 


Fig. 21.19

**Solution**

Fig. 21.20 shows the conditions of the problem.

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$2.5 = 10 \left( 1 + \frac{V_{GS}}{5} \right)^2$$

$$\text{or } 1 + \frac{V_{GS}}{5} = \sqrt{2.5/10} = 0.5$$

$$\text{or } V_{GS} = -2.5V$$

$$\begin{aligned} \text{Now, } V_2 &= \frac{V_{DD}}{R_1 + R_2} \times R_2 \\ &= \frac{30}{1000 + 500} \times 500 = 10V \end{aligned}$$

$$V_2 = V_{GS} + I_D R_S$$

$$\text{or } 10V = -2.5V + 2.5mA \times R_S$$

$$\therefore R_S = \frac{10V + 2.5V}{2.5mA} = \frac{12.5V}{2.5mA} = 5 \text{ K}\Omega$$

 


Fig. 21.20

**21.16. Voltage Gain of JFET Amplifier**

Fig. 21.21 shows a typical circuit of a JFET amplifier. The JFET is self-biased by using the biasing network  $R_S - C_S$ . The d. c. component of the drain current flowing through the source-biasing resistance  $R_S$  produces the desired bias voltage. The capacitor  $C_S$  bypasses the a.c. component of drain current. It may be noted that biasing circuit is similar to the cathode bias for a vacuum tube. The value of  $R_S$  can be determined from the following relation :

$$R_S = \frac{V_{GS}}{I_D}$$

where

$V_{GS}$  = voltage drop across  $R_S$  and  $I_D$  = current through  $R_S$

 


Fig. 21.21

Like a vacuum tube, a *JFET* is a voltage driven device. Therefore, the voltage gain of a *JFET* amplifier can be determined in the same manner as for a vacuum tube.

∴ Voltage gain of *JFET* amplifier,

$$A_v = \frac{\mu R_L}{r_d + R_L}$$

Since  $\mu = r_d \times g_{fs}$  ∴  $A_v = \frac{r_d g_{fs} R_L}{r_d + R_L}$

If  $r_d \gg R_L$ , then the latter can be neglected as compared to the former.

∴ Voltage gain,  $A_v = \frac{r_d g_{fs} R_L}{r_d}$  or  $A_v = g_{fs} \times R_L$

**Example 21.9.** The transconductance of a *JFET* used in a voltage-amplifier circuit is 3000  $\mu\text{mhos}$  and the load resistance is 10  $\text{k}\Omega$ . Calculate the voltage amplification of the circuit assuming that  $r_d \gg R_L$ .

**Solution.**

$$g_{fs} = 3000 \mu\text{mhos} = 3000 \times 10^{-6} \text{ mho} \quad \text{and} \quad R_L = 10 \text{ k}\Omega = 10,000 \Omega$$

As  $r_d \gg R_L$ ,

$$\therefore A_v = g_{fs} R_L = (3000 \times 10^{-6}) \times (10,000) = 30$$

**Example 21.10** In the *JFET* circuit shown in Fig 21.22, find (i)  $V_{DS}$  and (ii)  $V_{GS}$ .

**Solution.**

 


Fig. 21.22

$$V_{DS} = V_{DD} - I_D (R_D + R_S) = 30 - 2.5\text{mA} (5 + 0.2) = 30 - 13 = 17\text{V}$$

$$V_{GS} = -I_D R_S = -(2.5 \times 10^{-3}) \times 200 = -0.5\text{V}$$

**Example 21.11.** Figure 21.23 shows two stages of *JFET* amplifier. The first stage has  $I_D = 2.15\text{mA}$  and the second stage has  $I_D = 9.15\text{mA}$ . Find the d.c. voltage of drain and source of each stage w.r.t. ground.

**Solution**

Voltage drop in 8.2 $\text{k}\Omega$

$$= 2.15\text{mA} \times 8.2\text{k}\Omega = 17.63\text{V}$$

D.C. Potential of drain of first stage w.r.t. ground



$$V_D = V_{DD} - 17.63 = 30 - 17.63 = 12.37V$$

 


Fig. 21.23

D.C. potential of source of first stage to ground

$$V_S = I_D R_S = 2.15mA \times 0.68K\Omega = 1.46V$$

Voltage drop in  $2K\Omega = 9.15mA \times 2K\Omega = 18.3V$

D.C. potential of drain of second stage to ground

$$V_D = V_{DD} - 18.3 = 30 - 18.3 = 11.7V$$

D.C. Potential of source of second stage to ground

$$V_S = I_D R_S = 9.15mA \times 0.22K\Omega = 2.01V$$

## 21.17. JFET Applications

The high input impedance and low output impedance and low noise level make *JFET* far superior to the bipolar transistor. Some of the circuit applications of *JFET* are :

 


Fig. 21.24

(i) **As a buffer amplifier.** A buffer amplifier is a stage of amplification that isolates the preceding stage from the following stage. Because of the high input impedance and low output impedance, a *JFET* can act as an excellent buffer amplifier (See Fig. 21.24). The high input impedance of *JFET* means light loading of the preceding stage. This permits almost the entire output from first stage to appear at the buffer input. The low output impedance of *JFET* can drive heavy loads (or small load resistances). This ensures that all the output from the buffer reaches the input of the second stage.